

Computer Organization Final Project

Simple CPU

Design Description (1/3)

- An arithmetic logic unit (ALU) is a digital electronic circuit that performs arithmetic and bitwise logical operations on integer binary numbers. In order to increase clock frequency and throughputs, pipeline technology can be used.
- In this project, a string of instructions will be given. Your job is to decode these instructions and execute. You should try to design a simple 16-bits CPU with 16 registers.

Design Description (2/3)

- The following is the basic required instruction set: (similar to MIPS)

| Type | Format (19 bits) | | | | |
|-----------|------------------|-------------|-------------|--------------------|---------------|
| Logic | opcode (3 bits) | rs (4 bits) | rt (4 bits) | rd (4 bits) | func (4 bits) |
| Operation | opcode (3 bits) | rs (4 bits) | rt (4 bits) | rd (4 bits) | rl (4 bits) |
| Immediate | opcode (3 bits) | rs (4 bits) | rt (4 bits) | immediate (8 bits) | |

Design Description (3/3)

- Register s(rs), Register t(rt), Register d(rd) and Register l(rl) represent the address of registers. Since the instruction takes 4 bits to store the address, it means we have 16 registers, from r0 to r15. Each register reserve 16 bits to store data, e.g. rs = 4'b0000 means one of operands is “r0”. rt = 4'b0101 means one of operands is “r5”, and so on. And the outputs are corresponding to the registers, ex: out = r0 when we check your answer.
- There will be a 8192*16 data memory in this project. You can access this memory according to the instruction.

Instruction

| Function | Meaning | Instruction Binary Encode |
|----------|--|---------------------------|
| AND | $rd = rs \& rt$ (bit wise) | 000-ssss-tttt-dddd-0000 |
| OR | $rd = rs \mid rt$ (bit wise) | 000-ssss-tttt-dddd-0001 |
| XOR | $rd = rs \wedge rt$ (bit wise) | 000-ssss-tttt-dddd-0010 |
| ADD | $rd = rs + rt$ | 000-ssss-tttt-dddd-0011 |
| SUB | $rd = rs - rt$ | 000-ssss-tttt-dddd-0100 |
| MULT | $\{rd, rl\} = rs * rt$ | 001-ssss-tttt-dddd-llll |
| SQUARE | $\{rd, rl\} = rs^2$ | 010-ssss-tttt-dddd-llll |
| ADDI | $rt = rs + \text{immediate}$ (sign) | 011-ssss-tttt-iiii-iiii |
| SUBI | $rt = rs - \text{immediate}$ (sign) | 100-ssss-tttt-iiii-iiii |
| STORE | $\text{Memory}[rs[12:0] + \text{immediate} \text{ (sign)}] = rt$ | 101-ssss-tttt-iiii-iiii |
| LOAD | $rt = \text{Memory}[rs[12:0] + \text{immediate} \text{ (sign)}]$ | 110-ssss-tttt-iiii-iiii |

Example

- `instruction[18:0] = 19h'0_1230`

`opcode = 0, rs = 1, rt = 2, rd = 3, func = 0`



`r3 = r1 & r2`

- `instruction[18:0] = 19h'1_2345`

`opcode = 1, rs = 2, rt = 3, rd = 4, rl = 5`



`{r4, r5} = r2 * r3`

- `instruction[18:0] = 19h'3_45ff`

`opcode = 3, rs = 4, rt = 5, immediate = (-1)`



`r5 = r4 + (-1)`

- `instruction[18:0] = 19h'5_6701`

`opcode = 5, rs = 6, rt = 7, immediate = 1`



`Memory[r6[12:0] + 1] = r7`

- `instruction[18:0] = 19h'6_78ef`

`opcode = 6, rs = 7, rt = 8, immediate = 127`



`r8 = Memory[r7[12:0] + 127]`

Inputs

- All input signals will be **synchronized** at **negative edge** of the clock.

| Input | Bit Width | Definition and Description |
|-------------|-----------|---|
| clk | 1 | Positive edge trigger clock. |
| rst_n | 1 | Asynchronous active- low reset. |
| in_valid | 1 | instruction [18:0] is valid when in_valid is high. |
| instruction | 19 | As above. |
| MEM_out | 16 | When WEN is high, you can load data MEM_out [15:0] from memory. |

Outputs

| Output | Bit Width | Definition and Description |
|---------------------|-----------|---|
| busy | 1 | 1. busy should be low if you want to get the next instruction[18:0] . 2. If output port busy is low, the next instruction[18:0] and in_valid will be given immediately and stay one cycle. 3. As long as busy is low, instruction[18:0] will be sent as input every cycle. |
| out_valid | 1 | out_valid is high when you want to output your answer. We will check your answer when your out_valid is high. |
| out0 ~ out15 | 16 | out0[15:0] ~ out15[15:0] are synchronous to the positive edge of clk , and TA's pattern will sample your result at the following negative edge of clk . |
| WEN | 1 | Write Enable Negative is an input signal of memory. When WEN is high, you can load data from memory. When WEN is low, you can write data into memory. |
| ADDR | 13 | Memory address. |
| MEM_in | 16 | When WEN is low, MEM_in[15:0] will be written into memory. |


Specifications (1/2)

- Top module name : SCPU (File name : SCPU.v)
- Input pins: clk, rst_n, in_valid, instruction[18:0], MEM_out[15:0]
- Output pins: busy, out_valid, out0[15:0] ~ out15[15:0], WEN, ADDR[12:0], MEM_in[15:0].
- It is an **asynchronous** active-**low** reset and **positive** edge clk architecture.
- The reset signal would be given only once at the beginning of the simulation.

Specifications (2/2)

- All output signals should be reset after the reset signal is asserted.
- All of data in registers are **signed** number, including your output.
- The busy should be only kept high within 10 cycles.
- The rd won't be equal to rl when doing MULT and SQUARE.
- The first sixteen instructions are LOAD for out0 ~ out15.
- Overflow is allowed in your design.


Block Diagram

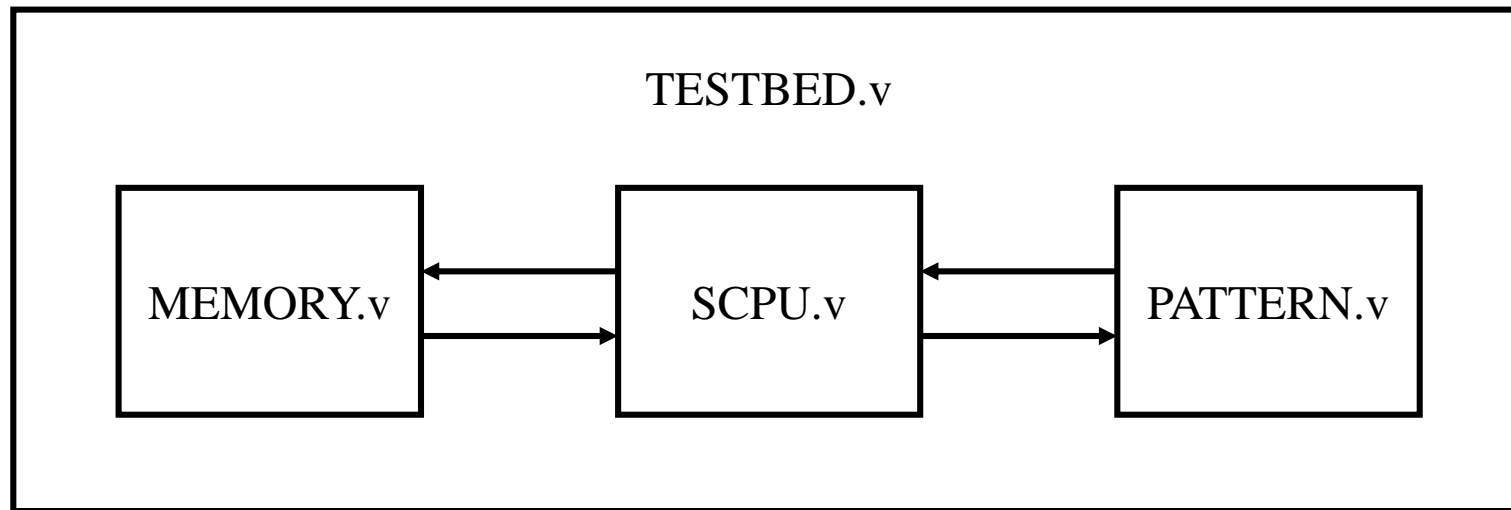


Grading Policy

- Function Validity: 75%
- Pipeline: 10% (Without using **busy**)
- Execution Cycles: 15% (You will get full score in this part if you use pipeline architecture)
- Please upload “SCPU_studentID.v” on New e3 platform
- Due Date: 23:59, January 12, Sunday, 2020
- If you have a late submission, you can only get 80% of your original score.

Example Waveform (Pipeline)

 

Example Waveform (Pipeline)

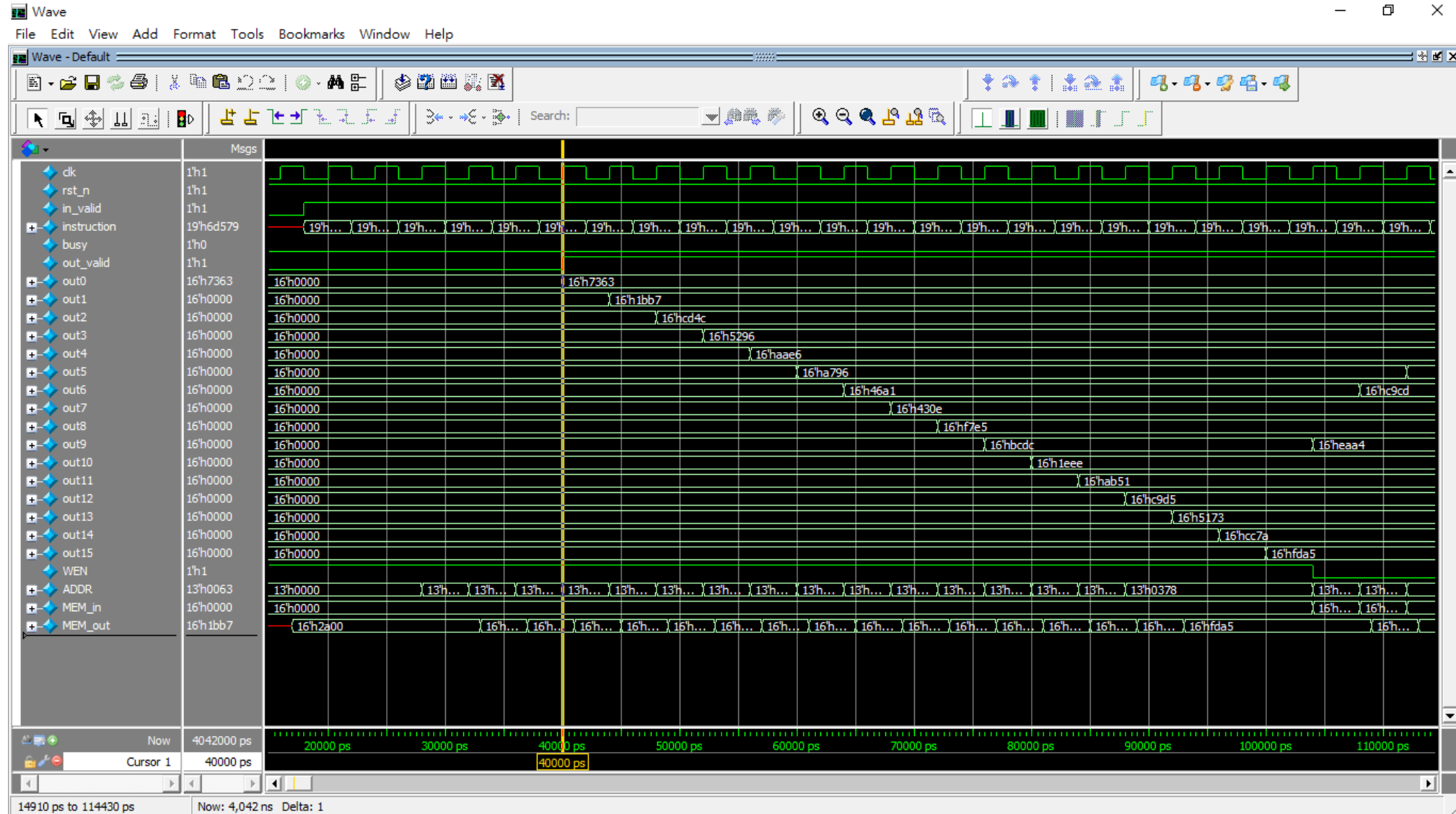

Example Waveform (With busy)

